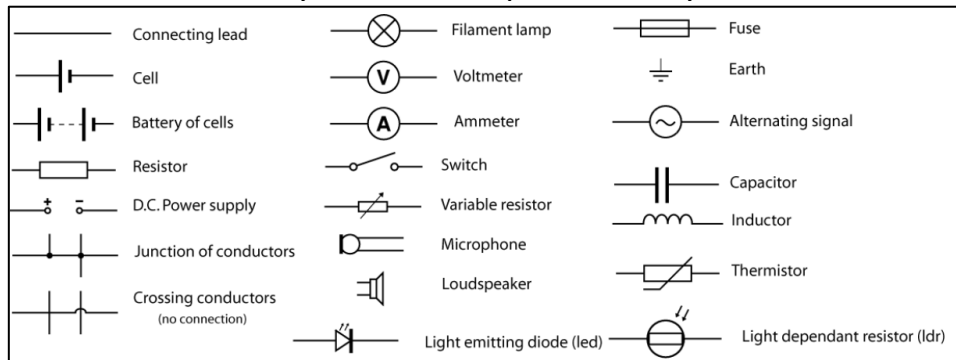


Power Failure - Bonus task


Name - _____

Can you find some of the components below in the walkie talkie circuit diagram?

How many of each component can you find?



Walkie Talkie Circuit Diagram

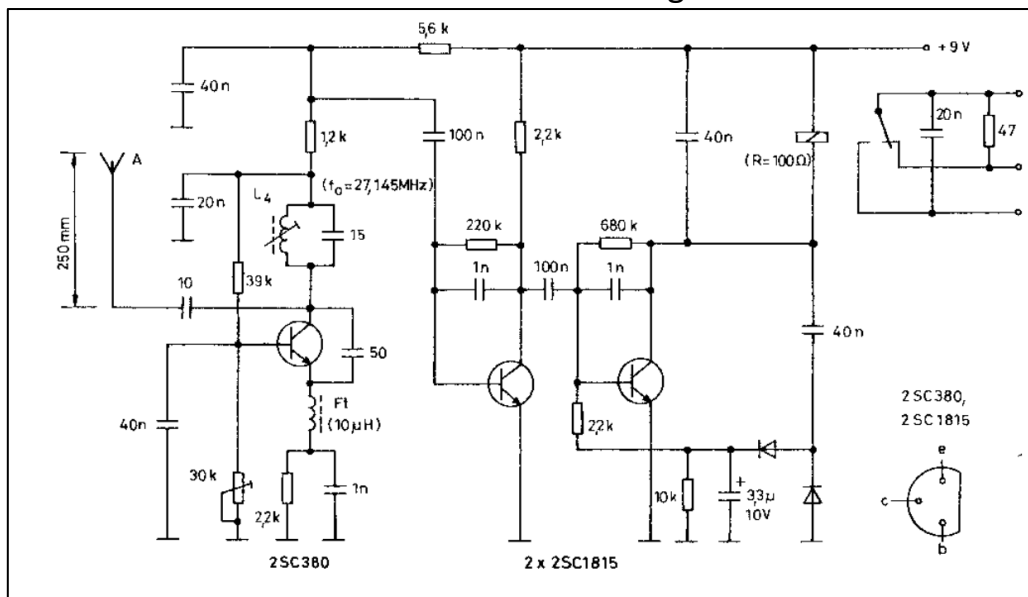

Component Name	Number		Component Name	Number